Test Bench Simulation Results

A plus B:

+> /testbench/a	4	4	28	-95	-44
+> /testbench/b	16	16	-75	9	-70
+> /testbench/c	0000	0000			
	20	20	-47	-86	-114

Increment A by 1:

- → /testbench/a	4	4	28	-95	-44
⊥ -♦ /testbench/b	16	16	-75	9	-70
+	0001	0001			
- → /testbench/f	5	5	29	-94	-43

A minus B:

-	4	4	28	-95	-44)
	16	16	-75	9	-70	
+> /testbench/c	0010	0010				
- → /testbench/f	-12	-12	103	-104	26	

Decrement A by 1:

+- /testbench/a	4	4	28	-95	-44
+- /testbench/b	16	16	-75	9	-70
+> /testbench/c	0011	0011			
 → /testbench/f	3	3	27	-96	-45

A times B:

≖ –♦ /testbench/a	4	4	28	161	212
- → /testbench/b	16	16	181	9	186
- → /testbench/c	0100	0100			
+- /testbench/f	64	64	5068	1449	39432

Minimum of A and B:

+ /testbench/a	4	4	28	-44	-95
+/b	16	16	-75	-70	-95
+> /testbench/c	0101	0101			
+- /testbench/f	4	4	-75	-70	-95

Maximum of A and B:

-	4	4	28	-44	33
 → /testbench/b	16	16	-75	-70	33
+> /testbench/c	0110	0110			
+-> /testbench/f	16	16	28	-44	33

Nadim Dib, Mohamad Katarnji

Circular right shift of A:

II - ✓ /testbench/a	00000100	00000100	00011101	10100001	11010100
x -<> /testbench/b	00010000	00010000	10110101	00001001	10111010
+ -♦ /testbench/c	1000	1000			
★→ /testbench/f7dowto0	00000010	00000010	10001110	11010000	01101010
	00000000	00000000	11111111		00000000

Circular left shift of A:

+	00000100	00000100	00011101	10100001	11010100
+- /testbench/b	00010000	00010000	10110101	00001001	10111010
IIIIIIIIIIIII	1001	1001			
IIIIIIIIIIIII	00001000	00001000	00111010	01000011	10101001
+ /testbench/f15dowto8	00000000	00000000			11111111

Right shift of A with feed in 0:

	00000100	00000100	00011101	10100001	11010100
∓ - /testbench/b	00010000	00010000	10110101	00001001	10111010
∓ - ♦ /testbench/c	1010	1010			
	00000010	00000010	00001110	01010000	01101010
+	00000000	00000000			

Left shift of A with feed in 0:

+	00000100	00000100	00011101	10100001	11010100
≖ –♦ /testbench/b	00010000	00010000	10110101	00001001	10111010
+- /testbench/c	1011	1011			
+- /testbench/f7downto0	00001000	00001000	00111010	01000010	10101000
+- /testbench/f15dowto8	00000000	00000000			11111111

Right shift of A with MSB replication:

- ✓ /testbench/a	00000100	00000100	00011101	10100001	11010100
∓ - → /testbench/b	00010000	00010000	10110101	00001001	10111010
+> /testbench/c	1110	1110			
+ /testbench/f7downto0	00000010	00000010	00001110	11010000	11101010
II Itestbench/f15dowto8	00000000	00000000		11111111	

Left shift of A with LSB replication:

+- /testbench/a	00000100	00000100	00011101	10100001	11010100
	00010000	00010000	10110101	00001001	10111010
	1101	1101			
+> /testbench/f7downto0	00001000	00001000	00111011	01000011	10101000
	00000000	00000000			11111111